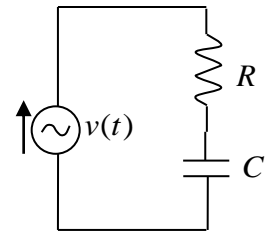


## ENGR 1990 Engineering Mathematics


### Homework #5 – Application of Complex Numbers in Electrical Engineering

1. A voltage  $v(t) = 110 \cos(120\pi t + \pi/3)$  volts is applied to the RC series circuit with  $R = 80 \Omega$  and  $C = 50 \mu\text{f}$ . Given that the total impedance is  $Z = Z_R + Z_C$ , find



- $Z$  in both rectangular and polar form
- $I$  the complex current in both rectangular and polar form
- $i(t)$  the current as a function of time

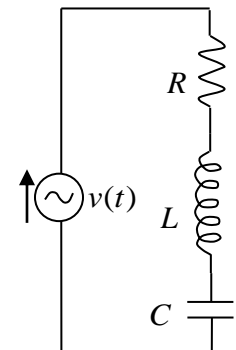
2. A voltage  $v(t) = 110 \cos(120\pi t)$  volts is applied to the RLC series circuit with  $R = 75 \Omega$ ,  $C = 40 \mu\text{f}$ , and  $L = 300 \text{ mH}$ . Given that the total impedance is  $Z = Z_R + Z_C + Z_L$ , find



- $Z$  in both rectangular and polar form
- $I$  the complex current in both rectangular and polar form
- $i(t)$  the current as a function of time

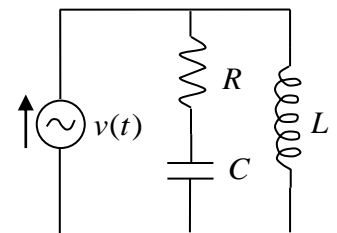3. A voltage  $v(t) = 110 \cos(120\pi t)$  volts is applied to the RLC parallel circuit with  $R = 100 (\Omega)$ ,  $C = 35 \mu\text{f}$ , and  $L = 500 \text{ mH}$ . Given that the


equivalent impedance is  $Z_{eq} = \frac{(Z_R + Z_C)Z_L}{(Z_R + Z_C) + Z_L}$ , find



- $(Z_R + Z_C)$  and  $Z_L$  in both rectangular and polar form
- $Z_{eq}$  the equivalent impedance in polar form

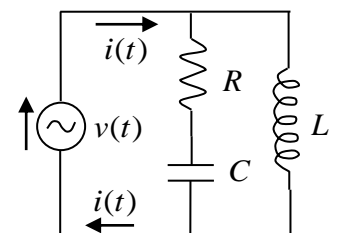4. A voltage  $v(t) = 110 \cos(120\pi t + \pi/3)$  volts is applied to the RLC parallel circuit with  $R = 200 (\Omega)$ ,  $C = 25 \mu\text{f}$ , and  $L = 800 \text{ mH}$ . Given

that the equivalent impedance is  $Z_{eq} = \frac{(Z_R + Z_C)Z_L}{(Z_R + Z_C) + Z_L}$ , find



- $Z_{eq}$  in polar form
- $I$  the complex current in polar form
- $i(t)$  the total current as a function of time

Impedances for AC circuit elements:  $Z_R = R$ ,  $Z_C = \frac{-j}{\omega C}$ , and  $Z_L = j\omega L$

Complex form of Ohm's Law:  $V = IZ$