


# Elementary Engineering Mathematics

## Exercises #5 – Application of Complex Numbers in Electrical Engineering

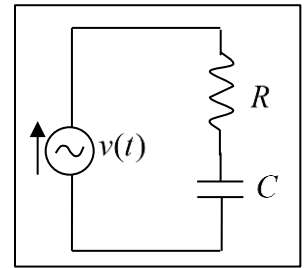1. A voltage  $v(t) = 110 \cos(120\pi t + \pi/3)$  volts is applied to the RC series circuit with

$R = 80 \Omega$  and  $C = 50 \mu f$ . Given that the total impedance is  $Z = Z_R + Z_C$ , find

- $Z$  in both rectangular and polar form
- $I$  the complex current in both rectangular and polar form
- $i(t)$  the current as a function of time




2. A voltage  $v(t) = 110 \cos(120\pi t)$  volts is applied to the RLC series circuit with

$R = 75 \Omega$ ,  $C = 40 \mu f$ , and  $L = 300 \text{ mh}$ . Given that the total impedance is the sum

$Z = Z_R + Z_C + Z_L$ , find

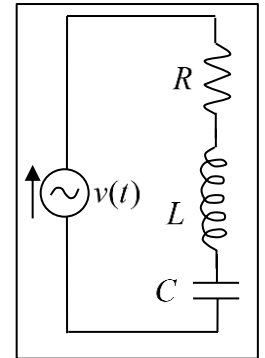
- $Z$  in both rectangular and polar form
- $I$  the complex current in both rectangular and polar form
- $i(t)$  the current as a function of time



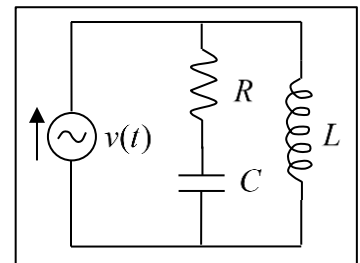3. A voltage  $v(t) = 110 \cos(120\pi t)$  volts is applied to the RLC parallel circuit with  $R = 100 (\Omega)$ ,  $C = 35 \mu f$ , and  $L = 500 \text{ mh}$ . Given that the equivalent

impedance is given by the equation  $Z_{eq} = \frac{(Z_R + Z_C)Z_L}{(Z_R + Z_C) + Z_L}$ , find


- $(Z_R + Z_C)$  and  $Z_L$  in both rectangular and polar form
- $Z_{eq}$  the equivalent impedance in polar form



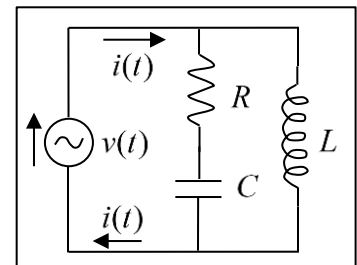4. A voltage  $v(t) = 110 \cos(120\pi t + \pi/3)$  volts is applied to the RLC parallel circuit with  $R = 200 (\Omega)$ ,  $C = 25 \mu f$ , and  $L = 800 \text{ mh}$ . Given that the

equivalent impedance is  $Z_{eq} = \frac{(Z_R + Z_C)Z_L}{(Z_R + Z_C) + Z_L}$ , find

- $Z_{eq}$  in polar form
- $I$  the complex current in polar form
- $i(t)$  the total current as a function of time



Impedances for AC circuit elements:  $Z_R = R$ ,  $Z_C = \frac{-j}{\omega C}$ , and  $Z_L = j \omega L$

Complex form of Ohm's Law:  $V = IZ$